

ALLAMA IQBAL OPEN UNIVERSITY, ISLAMABAD
(Department of Computer Science)

WARNING

1. **PLAGIARISM OR HIRING OF GHOST WRITER(S) FOR SOLVING THE ASSIGNMENT(S) WILL DEBAR THE STUDENT FROM AWARD OF DEGREE/CERTIFICATE, IF FOUND AT ANY STAGE.**
2. **SUBMITTING ASSIGNMENTS BORROWED OR STOLEN FROM “AIOU PLAGIARISM POLICY”.**

Course: Digital Logic Design (3409)
Level: Bachelor

Semester: Autumn, 2012
Total Marks: 100

ASSIGNMENT No. 1

Note: All questions are compulsory and carry equal marks.

- Q. 1 a) Convert the following binary numbers to decimal system:
i) 10111101 ii) 1110100
- b) Perform the subtraction with the following decimal numbers using 1's complements and 2's complements.
i) 1010100 – 1000100 ii) 11101011 – 1001110
- Q. 2 a) Explain the process of following conversions with examples:
i) Binary to Octal and Hexadecimal
ii) Octal and Hexadecimal to Binary
- b) Differentiate Map method and Tabulation method in detail. Also discuss difference between Adder and Subtractor.
- Q. 3 a) Expand the following Boolean functions into their canonical forms:
 $F_1(A, B, C) = A'B + C$ $F_2(A, B, C) = AB + A'C + AB'C$
- b) What are logic gates? Differentiate the following gates AND, OR, NAND and NOR.
- Q. 4 a) Design a combinational circuit that accepts a three-bit number and generates an output binary number equal to the square of the input number.
- b) Implement the Boolean function:
 $F = AB'CD' + A'BCD + AB'C'D + A'BC'D$
With exclusive-OR and AND gates.

Q. 5 Write a note on each of the following:

- a) Binary Logic and ICs
- b) Gates
- c) Boolean Functions
- d) Tabulation Method

ASSIGNMENT No. 2

Total Marks: 100

Q. 1 a) Design a BCD-to-excess-3 code convertor with a BCD-to-decimal decoder and four OR gates.

b) Differentiate between full adder and half adder.

Q. 2 a) Show the logic diagram of a clocked RS flip-flop with four NAND gates.

b) Design a counter with the following binary sequence: 0, 1, 3, 7, 6, 4 and repeat. Use T flip-flops.

Q. 3 a) Differentiate Ripple Counters and Synchronous Counters with the help of an example.

b) Differentiate between multiplexer and de-multiplexer.

Q. 4 a) What is the difference between serial and parallel transfer? What type of register is used in each case?

b) Draw the interconnection of I^2L gates to form a 2x4 decoder.

Q. 5 Write a note on each of the following:

- a) Memory
- b) Register Counter
- c) Decimal Adder
- d) CMOS

3409 Digital Logic Design

Credit Hours: 4 (4+0)

Recommended Book:

Digital Logic Design by Morris Mano

Course Outlines:

- Unit-1: Binary System**
Binary Numbers Based Conversion of Octal, Hexadecimal and Binary, Complements, Binary Codes, Binary Logic and ICs
- Unit-2: Boolean Algebra and Logic Gates**
Definitions, Theorems and Properties, Boolean Functions, Canonical and STD Forms, other Logical Properties, Gates
- Unit-3: Simplification of Boolean Function**
Map Method, NAND and NOR Implementation, Tabulation Method, Prime Implement
- Unit-4: Combination Logic**
Design Procedure, Adder, Subtractors, Code Conversation Analysis Procedure, NAND and NOR Functions, Ex-OR and Ex-NOR Function
- Unit-5: Combination Logic with MSI and LSI**
Binary Parallel Adder, Decimal Adder, BCD Counter, Magnitude Compactor, Decoders, Demultiplexers, Encoder, Multiplexer, ROM, PLA
- Unit-6: Sequential Logic**
Introduction, Flip Flop, Triggering, State Reduction Excitation Table, Design Procedure, Design of Counter
- Unit-7: Register, Counter, and Memory Unit**
Register Counter, Timing Sequence, Memory Unit
- Unit-8: Asynchronous Sequential Logic**
Analysis Procedure, Circuits with Latches, Design Procedure, Reductions of State and Flow Tables, Race Free State Assignment
- Unit-9: Digital Integrated Circuits**
Bipolar Transistor Characteristics, RTL and DTL Circuits, Transistor, Transistor Logic, Emitter Coupled Logic (ECL), Metal Oxide Semiconductor (MOS), CMOS